

B. TECH.
(SEM I) THEORY EXAMINATION 2018-19
ELECTRONICS ENGINEERING

Time: 3 Hours**Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**

- a) Write some applications of P-N junction diode.
- b) What is meant by peak repetitive forward current
- c) What are the requirements of biasing circuits? Explain.
- d) What is early effect?
- e) Write the advantages of JFET over BJT.
- f) What is meant by saturation region
- g) Write the application of CRO
- h) What are the disadvantages of DVM?
- i) Define the truth table
- j) What are the basic laws of Boolean algebra?

SECTION B**2. Attempt any three of the following: 10 x 3 = 30**

- a) Explain the Diffusion capacitance and transition capacitance of a PN –diode.
- b) Explain the input and output characteristics of a transistor in CB configurations.
- c) Explain the construction and working of enhancement type MOSFET.
- d) Explain the working of digital voltmeter with the help of block diagram.
- e) Simplify the given expression using the Boolean algebra method
 $BD + B(D+E) + \bar{D} (D+F)$

SECTION C**3. Attempt any one part of the following: 10 x 1 = 10**

- a) Draw a circuit diagram of a bridge rectifier. Discuss the voltage regulation and efficiency of the circuit.
- b) A half wave rectifier rectifies an alternating voltage of 325-volt peak value and the diode has a forward resistance of 100 Ω . The value of load resistance is 1000 Ω . Determine the following: peak value, dc power output, AC input power, efficiency of the rectifier.

4. Attempt any one part of the following: 10 x 1 = 10

- a) What are the characteristics of an ideal operational amplifier? Explain an inverting amplifier.
- b) Draw the circuit diagram of JFET as an amplifier and explain its working.

5. Attempt any one part of the following: 10 x 1 = 10

- a) Draw a fixed bias circuit and obtain the value of d.c. voltages and currents in the circuit.
- b) What are the factors responsible for the instability of operating point? Also explain the various methods of improving stability.

6. Attempt any *one* part of the following: 10 x 1 = 10
a) Draw the block diagram of a CRO and briefly explain the function of each block.
b) Explain the working of digital multimeter with the help of block diagram.
7. Attempt any *one* part of the following: 10 x 1 = 10
a) Prepare k map for the following:
$$f = A + B + \overline{C}$$

b) Explain how multiplication and subtraction performed in digital systems. Explain the concept of universal gates.