

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2302

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B.Tech.

(SEM. II) THEORY EXAMINATION 2010-11

ELECTRICAL ENGINEERING

Time : 3 Hours

Total Marks : 100

Note :- ALL sections are compulsory.

SECTION—A

1. All parts are compulsory. All questions carry equal marks :— **10×2=20**

(a) The power consumed in an inductive circuit will be :

(i) $v_i \cos \theta$ (ii) $v_i \sin \theta$ (iii) v_i

(iv) none of these

(b) An ideal voltage source should have:

(i) large e.m.f.

(ii) small e.m.f.

(iii) zero resistance

(iv) none of these

(c) Superposition theorem is applicable for :

(i) Linear circuits only

(ii) Non-linear circuits only

(iii) Linear and non-linear circuits both

(iv) None of these

(d) The current through a series RLC circuit under resonance condition will be

(i) V/R (ii) V/X_c (iii) V/X_L

(iv) None of these

- (e) For a 3-phase load balanced condition, each phase has the same value of
- (i) impedance (ii) resistance
 - (iii) power factor (iv) all of these
- (f) The is an integrating type instrument.
- (i) Moving iron ammeter
 - (ii) Moving coil voltmeter
 - (iii) Dynamometer wattmeter
 - (iv) Induction type energy meter
- (g) When voltage is transferred from primary to secondary then it is
- (i) multiplied by K^2 (ii) multiplied by K
 - (iii) divided by K^2 (iv) divided by K
- (h) Stray losses are sum of :
- (i) Iron and mechanical losses
 - (ii) Copper and iron losses
 - (iii) Copper and mechanical losses
 - (iv) None of these
- (i) If N_s is the synchronous speed, N is the rotor speed and S is the slip then the relation is :
- (i) $N_s = (1 - S)N$ (ii) $N = S \cdot N_s$
 - (iii) $N = (S - 1)N_s$ (iv) None of these
- (j) An electrical installation is earthed for :
- (i) safety to personnel
 - (ii) fire protection
 - (iii) protection against electric shock
 - (iv) all of these

SECTION—B

2. Attempt any **THREE** parts of the following. All questions carry equal marks :— **10×3=30**

- (a) Write the statement of Norton's theorem and discuss it with help of example.

A network has the configuration shown in Fig. 1. All resistance values are expressed in ohms.

- (i) Find the current through R_L when it takes on values of 10, 50, and 200 Ω using Thevenin's theorem.
- (ii) Determine the value of R_L corresponding to which there a maximum power is transferred to the load resistor. Compute this maximum power.

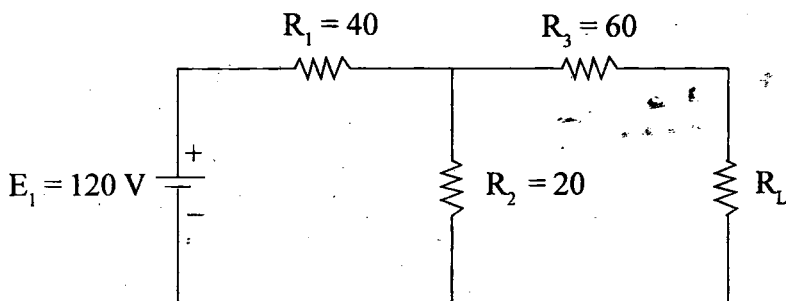


Fig. 1

- (b) How are settling time and time constant related in a first-order linear circuit? Also derive the step response of (i) R_L series circuit (ii) R_C series circuit.
- (c) Explain the working of a transformer with the derivation of the e.m.f. equation for a transformer. Also discuss the losses in the transformer.

- (d) Derive the expression of torque for D.C. Motor. Also discuss the characteristics of D.C. shunt motor.

A 6 pole lap wound D.C. generator has 720 conductors; a flux of 80 m weber/pole is driven at 1000 rpm. Find the generated e.m.f.

SECTION—C

Note :—All questions are compulsory. All questions carry equal marks. 10×5=15

3. Attempt any **TWO** parts of the following. All questions carry equal marks :—

- (a) Derive the expression for Q-factor in the R-L-C- parallel circuit.
- (b) Define power factor. Also discuss the reasons for low power factor and ways to improve it.
- (c) In Fig. 2 compute the voltage required between terminal a-b so that a voltage drop of 45 V occurs across 15 ohm resistor.

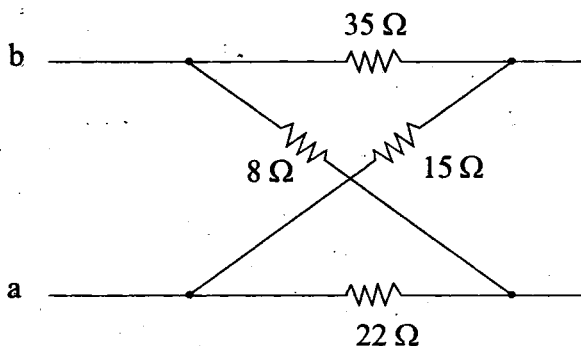


Fig. 2

4. Attempt any **TWO** parts of the following. All questions carry equal marks :—
- (a) Discuss the construction and working principle of PMMC type measuring instruments.
 - (b) Explain the two wattmeter method to determine the power in three phase system.
 - (c) For the given circuit find the (1) Line currents (2) Phase currents and (3) Power consumed.

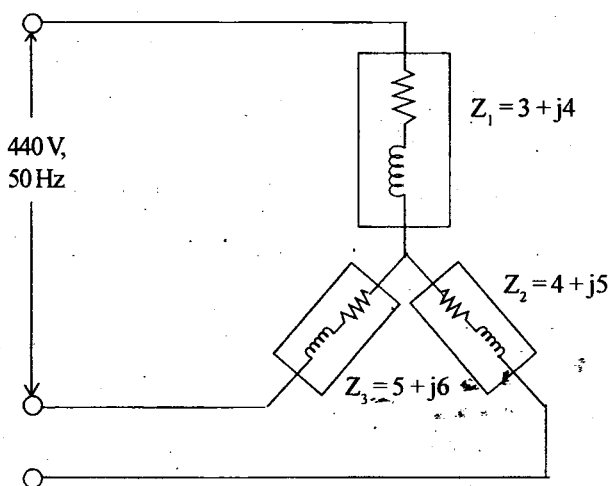


Fig. 3

5. Attempt any **TWO** parts of the following. All questions carry equal marks.
- (a) Derive the expression for efficiency of transformer. Also find out the condition of maximum efficiency.
 - (b) Explain the slip-torque characteristics of three phase induction motor.

- (c) Discuss the principle of operation of a single phase induction motor. Also write its applications.
6. Attempt any **TWO** parts of the following. All questions carry equal marks :—
- Describe the working principle of d.c. series motor and draw its various characteristics.
 - Discuss the working principle of a three-phase synchronous machine. Also differentiate synchronous motor from induction motor.
 - Explain the squirrel cage rotor and phase wound rotor in induction motor.
7. Attempt any **TWO** parts of the following. All questions carry equal marks.
- Explain the analogy between electric and magnetic circuit with AC excitation. Also determine the power factor for the given circuit in Fig. 4.

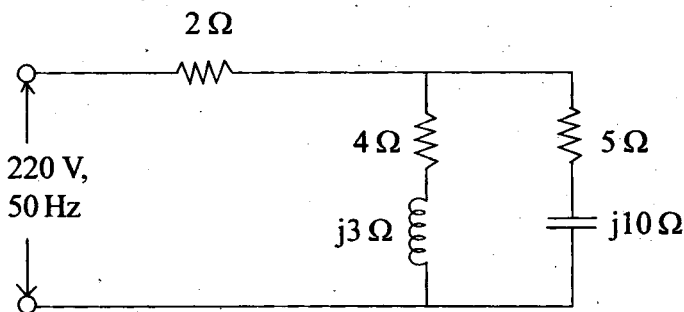


Fig. 4

(b) Discuss the following :—

- (i) Form factor, peak factor, permeability, flux density.
- (ii) Use of shunt and multipliers in measuring instruments.

(c) Describe the basic fundamentals of standard transmission and distribution of voltages. Also briefly discuss the concept of grid.