

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0323

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.
(SEM. III) THEORY EXAMINATION, 2012-13
DIGITAL ELECTRONICS

Time : 3 Hours]

[Total Marks : 100

SECTION – A

1. Attempt **all** parts : **10 × 2 = 20**
- (a) What is the largest binary number that can be expressed with (i) 14 bits and (ii) 10 bits ?
- (b) Convert $(247.36)_8 = (?)_{16}$.
- (c) If the number of states of a counter is 8, then find the number of flip-flops required for it.
- (d) Simplify the following Boolean expression.
$$F = (AB + \bar{A}B + \bar{A}\bar{B})$$
- (e) What do you mean by Edge-triggering & Level-triggering in flip-flops ?
- (f) A 3-bit synchronous counter uses flip-flops with propagation delay time 20 ns each. Determine the maximum possible time required for change of state.
- (g) What is the maximum number of product terms in a minimal sum of products form of a function of n Boolean variables ?
- (h) What problem could occur when the counter circuit is powered-up ? Give two possible general methods for overcoming the problem.
- (i) How many address lines and input-output data lines are needed in $2M \times 8$ memory unit ?
- (j) Define Primitive Flow Table ?
- (k) What is the difference between an internal state and a total state ?

SECTION – B

2. Attempt any **three** parts.**3 × 10 = 30**

(a) Given :

$$F = A \cdot B \cdot \bar{C} \cdot D + A \cdot C + B \bar{C} \cdot \bar{D} + \bar{B} \cdot C + \bar{A} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D$$

(i) Show using a K-map that F can be simplified to

$$F_1 = A \cdot B + \bar{A} \cdot \bar{B} + A \cdot C + B \cdot \bar{C} \cdot \bar{D}$$

(ii) Show that there are a total of four possible expressions for F.

(iii) Show F_1 can be implemented using NAND gates and draw the circuit diagram.

(b) Using four half-adders :

(i) Design a two-bit binary magnitude comparator.

(ii) Realize expression F using 8-to-1 multiplexer.

$$F = f(x, y, z) = \sum (1, 2, 4, 5, 7)$$

(c) Explain the working of a Master – Slave JK flip-flop with functional table and timing diagram. Show how race around condition of master-slave SR flip-flop is over come.

(d) Draw the Block Diagram, Data path and ASMD chart for a binary multiplier.

(e) Obtain a primitive flow table for a circuit with two inputs, x_1 and x_2 , and two outputs, z_1 and z_2 that satisfy the following four conditions.(i) When $x_1 x_2 = 00$, the output is $z_1 z_2 = 00$ (ii) When $x_1 = 1$, and x_2 changes from 0 to 1, the output is $z_1 z_2 = 01$ (iii) When $x_2 = 1$, and x_1 changes from 0 to 1, the output is $z_1 z_2 = 10$

(iv) Otherwise, the output does not change.

SECTION – C

Attempt **all** parts :**5 × 10 = 50**3. Attempt any **one** part :

(a) The state of 9 bit register is 111011010. What is its content if it represents

(i) Three decimal digits in BCD ?

(ii) Three decimal digits in the excess-3 code ?

(iii) Three decimal digits in the 8-4-2-1 code ?

(iv) A binary number ?

- (b) Simplify the Boolean function $F = A'B'C' + BC'D' + A'BCD' + AB'C'$ using four-variable k-map. Explain briefly Prime Implicants.

4. Attempt any **one** part :

- (a) (i) Design a BCD to Excess-3 Code Converter.
 (ii) Explain different types of RAM & ROM.
- (b) Implement the following Boolean function with a PLA
 (i) $F(A, B, C, D) = \sum(0, 2, 5, 7, 11, 14)$
 (ii) $F(A, B, C) = \sum(0, 3, 5, 7)$

5. Attempt any **one** part :

- (a) Design a Mealy and Moore state machines for the detection of sequence 0101.
 (b) A sequential circuit has two JK flip-flops A and B and input x . The circuit is described by the following flip-flop input equations.

$$J_A = Bx + B'y' \quad K_A = B'xy'$$

$$J_B = A'x \quad K_B = A + xy'$$

- (i) Derive the state equations $A(t+1)$ and $B(t+1)$ by substituting the input equations for the J and K variables.
 (ii) Draw the state diagram of the circuit.

6. Attempt any **one** part :

- (a) It is necessary to formulate the Hamming Code for four data bits D3, D5, D6 and D7, together with three parity bits P1, P2 and P4.
 (i) Evaluate the 7-bit composite code word for the data word 0010.
 (ii) Evaluate three check bits C4, C2 and C1 assuming no error.
 (iii) Assuming an error in bit D5 during writing into memory. Show how the error in the bit is detected and corrected.
- (b) (i) Derive the ROM programming table for the combinational circuit that squares a four-bit number.
 (ii) Minimize the number of product terms of part (i).

7. Attempt any **one** part :

- (a) Design a sequential 8-bit multiplier. You can assume that a 16-bit adder has been provided. The finite state control can be described by a state diagram.
- (b) Explain Hazards in Combinational & Sequential Circuits.
