

Number of Printed Pages — 5

EC-302**B.TECH.**

THIRD SEMESTER EXAMINATION, 2001-2002

SWITCHING THEORY & LOGIC DESIGN*Time—2 Hours**Total Marks—50***Note :** Answer *ALL* the questions.

1. Attempt any *Two* parts. All parts carry equal marks. 4×2

- (a) Simplify the Boolean function F in Sum-of-product using the don't - care conditions d :

$$F = B'C'D' + BCD' + ABCD'$$

$$d = B'CD' + ABC'D$$

- (b) Simplify the following Boolean function by means of the tabulation method :—

$$F(A, B, C, D) = \sum(4, 6, 7, 8, 9, 10, 11, 15)$$

- (c) The following Boolean Expression :

$BE + B'DE'$ is a simplified version of expression :—

$$A'BE + BCDE + BC'D'E + A'B'DE' + B'C'DE'$$

Are there any don't-care conditions ? If so, what are they ?

2. Attempt any *Four* parts. All parts carry equal marks. $3\frac{1}{2} \times 4$

- (a) (i) Find the decimal equivalent of the following binary numbers assuming signed magnitude representation of the binary number :—

(1) 001000

(2) 1111

- (ii) Write the procedure for the subtraction of two numbers with $(r-1)$'s complement.
- (b) Perform the subtraction with the following binary numbers using (1) 2's complement (2) 1's complement.
- (i) $11010 - 1101$
- (ii) $10010 - 10011$
- (c) Perform the subtraction with following decimal numbers using (1) 10's complement (2) 9's complement.
- (i) $5294 - 749$
- (ii) $27 - 289$
- (d) Implement the following function with a 4×1 multiplexer.

$$F(A, B, C) = \sum (1, 3, 5, 6)$$

- (e) Implement a full-adder circuit with a 3×8 decoder and two OR-gates.
- (f) What is Hazards ? How will you design a Hazard-free switching circuit ?
3. Attempt any *Four* parts. All parts carry equal marks. $3\frac{1}{2} \times 4$
- (a) How will you differentiate between combinational circuit and sequential circuit.
Consider a J-K' flip-flop, i.e. a J-K flip-flop with an inverter between external input K' and internal input K.
- (i) Obtain the flip-flop characteristic table.
- (ii) Obtain the characteristic equation.

- (b) Prepare the truth-table for the circuit of fig-3b and show that it acts as a T-flip-flop.

 


Figure-3b

- (c) A mod-3 counter (reset after every three pulses) is shown in fig-3c. The flip-flops used are master-slave J-K. Sketch the waveform of Q_0 and Q_1 when clock pulses are applied and verify its operation. Assume $Q_0 = Q_1 = 0$ initially.

 


Figure-3c

- (d) What is race-around condition ?

If \bar{Q} output of a D-type flip-flop is connected to D-input, it acts as a toggle switch, verify.

- (e) For the state diagram shown in figure-3e, obtain the state table and design the circuit using minimum number of J-K flip-flop.

 


Figure-3e

- (f) Design a 3-bit binary UP/DOWN counter with a direction control M. Use J-K flip-flop.
4. Attempt any *Four* parts. All parts carry equal marks. $3\frac{1}{2} \times 4$
- Explain the principle of constructing a Hamming error-correcting code. Construct a Seven-bit Hamming code for the 4-bit message 0100.
 - Explain the floating-point data representation for decimal number and binary number. When is a floating point number said to be normalized ?
 - What is the difference between asynchronous and synchronous circuits ? Represent the Octal number $(17.32)_8$ into floating point Octal number and floating point binary number.
 - Draw the basic model for fundamental mode circuits and explain.