



(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 131315**Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.Tech. (Semester-III)****SPL. THEORY EXAMINATION, 2014-15****SWITCHING THEORY LOGIC DESIGN***Time : 2 Hours]**[Total Marks : 50*1. Attempt any two parts:

6×2=12

- (a) An asynchronous sequential logic circuit is described by the following excitation and output function:

$$y = X_1 X_2 + (X_1 + X_2) Y$$

$$Z = y$$

Draw the logic diagram of the circuit. Also derive the transition table and output map.

- (b) (i) Explain a  $4 \times 1$  mux.

- (ii) Implement the logic expression

$$Y = \sum m(0, 1, 2, 3, 6, 7) \text{ using mux.}$$

131315]

(1)

[Contd...

(c) Minimize:

$$y = \sum m(0, 1, 2, 3, 5, 6, 7, 8, 14, 15) + d(4, 11, 13)$$

using tabular method.

2. Attempt any four parts: 4×4=16

(a) Draw and explain single-bit magnitude comparator.

(b) Draw and explain the SISO, SIPO register.

(c) Implement a full adder using decoder and two or gates.

(d) Write the canonical form of

$$Y = (A+B)(B+C)(A+C)$$

(e) Simplify the following Boolean function using K-map:

$$Y = \sum m(0, 1, 2, 3, 4, 6, 7, 9, 11, 13, 15) + d(8, 12)$$

3. Attempt all three parts: 4×3=12

(a) Convert the following:

(i)  $(ABC.75)_{16} = (?)_{10}$

(ii)  $(467.342)_8 = (?)_{10}$

(b) What is race around condition? How it can be avoided.

(c) Generate the hamming code for the word 11011.

131315]

(2)

1,650

131315]

(3)

1,650

4. Attempt any two parts: 4×2=10

(a) Design a universal shift register that performs HOLD, SHIFT RIGHT, SHIFT LEFT and LOAD.

(b) Write the steps for combinational circuit designing and design a circuit of three input which gives an high output whenever the sum of LSB and MSB bit is 1.

(c) Draw and explain 3-bit by 2-bit multiplier.

—x—