

Printed Pages: 4

NEE-302

(Following Paper ID and Roll No. to be filled in your
Answer Books)

Paper ID : 2012379

Roll No.

--	--	--	--	--	--	--	--	--	--

B.TECH.

Regular Theory Examination (Odd Sem-III), 2016-17

**ELECTRICAL MEASUREMENTS &
MEASURING INSTRUMENTS**

*Time : 3 Hours**Max. Marks : 100***Note: Attempt all Sections.****SECTION - A****1. Attempt All Parts of the following: (10×2=20)**

- i) Differentiate the terms "Static error" and "Limiting error".
- ii) Why the scale of moving iron instruments is usable over about 80° of its length? Explain.
- iii) Enlist the major advantages of instrument transformers in terms of extension of range.
- iv) How does a potential transformer differ from an ordinary power transformer?
- v) What do you understand by low, medium and high resistances?

302/12/2016/6280

(1)

[P.T.O.]

NEE-302

- vi) Calculate insulation resistance of a cable in which the voltage falls from 200 V to 160V in 20 sec. The capacitance is $0.3 \mu F$.
- vii) What is the term "standardization" in ac potentiometer.
- viii) Explain the significance of area of Hysteresis curve in magnetic measurement.
- ix) List different types of DVMs.
- x) Explain the various applications of CRO in measurement.

SECTION - B

Note: Attempt any FIVE Parts of the following: (5×10=50)

- 2. Discuss and analyse the error algebra in measurement systems.
- 3. An electrostatic voltmeter reading upto 2500 V is controlled by a spring with spring constant of 10×10^{-6} N-m/deg and has a full scale deflection of 80° . The capacitance at zero voltage is 10 pF. What is the capacitance when the pointer indicates 1 kV?
- 4. A wattmeter is rated at 10 A and 25 V. The current coil has a resistance of 0.06Ω and a reactance of 0.02Ω . The potential coil circuit may be assumed to be purely resistive having a resistance of 6250Ω . Find the errors due to two different connections of wattmeter coils. The

NEE-302

load is 10 A at p.f. of 0.174 lagging. The voltage across the load is 25V.

5. Define the following terms as used for instrument transformers:
- i) Rated current
 - ii) Nominal current
 - iii) Transformer ratio
 - iv) Nominal ratio
 - v) Turns ratio
 - vi) Burden
 - vii) Ratio correction factor
6. What are the problems associated with the measurement of low resistances and how are they Overcome in Kelvin's double bridge? Derive an expression for the unknown resistance in case of kelvin's double bridge.
7. Describe how magnetizing loss component of no-load current of a transformer can be determined by using a.c. Potentiometer.
8. With the help of block diagram explain the working of a harmonic analyzer.
9. Describe the construction and working of dual beam CRO using block diagram.

NEE-302**SECTION - C**

Note: Attempt any **TWO** Parts of the following: (2×15=30)

10. Explain the construction and working of single-phase electro-dynamometer type power factor meter. Prove that the deflection of moving system is equal to the phase angle of the system.
11. In an Anderson's bridge for measurement of inductance L_1 and resistance R_1 in the arm AB, arm CD and DA have resistances of 600Ω each and the arm CE has a capacitor of $1.0 \mu F$ capacitance. With an AC supply at 100 Hz supplied across A and C; balance is obtained with a resistance of 400Ω in an arm DE and 800Ω in an arm BC. Calculate the value of L_1 and R_1 .
12. Describe the Lloyd Fisher square for measurement of iron losses in a specimen of laminations. Also explain how corrections for resistance of wattmeter pressure coil resistance and resistance of secondary winding are applied.

