

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 121406

Roll No.

B.Tech.

(SEM. IV) THEORY EXAMINATION 2013-14

NETWORK ANALYSIS & SYNTHESIS

Time : 3 Hours

Total Marks : 100

Note :- Attempt **all** questions. Each question carries equal marks.1. Answer any **two** parts of the following : (10×2=20)

(a) (i) What do you mean by "GRAPH" and "ORIENTED GRAPH" in circuit theory? What are the advantages and disadvantages of graph theory approach over conventional approaches?

(ii) Derive the KCL and KVL using graph theory.

(b) The fundamental cut-set matrix is given as :

CUT-SET/ BRANCHES	TWIGS	LINKS
	1 2 3 4	5 6 7
C_1	1 0 0 0	-1 6 7
C_2	0 1 0 0	1 0 1
C_3	0 0 1 0	0 1 1
C_4	0 0 0 1	0 1 0

(i) Draw and explain the oriented graph of the network.

(ii) Determine the "INCIDENCE MATRIX" of the network.

(c) Consider the network shown in Fig. 1 and 2.

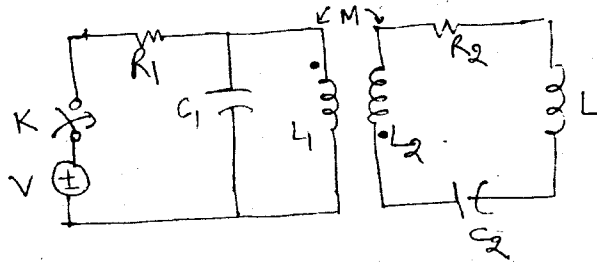


Fig. 1. network

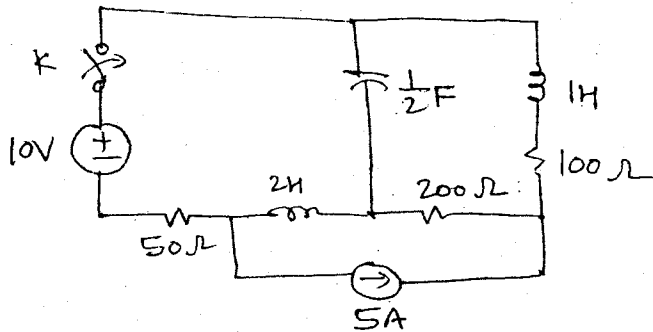


Fig. 2. network

Draw and explain the dual of the networks shown in Fig.(1) and (2).

2. Answer any two parts of the following : (10×2=20)

(a) Explain why "SUPER-POSITION THEOREM" is not applicable for power and energy verifications of a given networks ? Explain the following :

- LINEARITY PRINCIPLE
- HOMOGENEITY PRINCIPLE.

(b) Consider the network shown in Fig. 3.

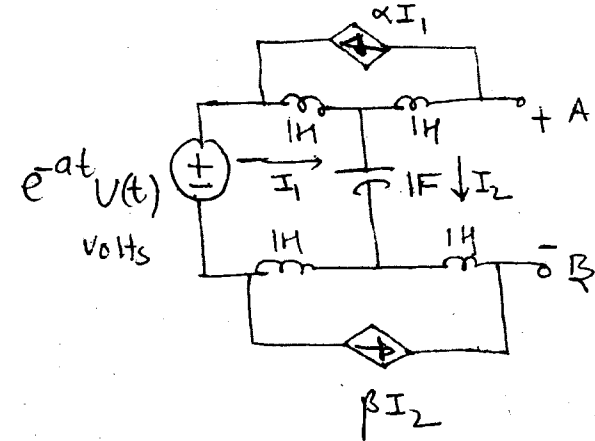


Fig. 3

Find the Thevenin's equivalent circuit across the AB-terminals of network. Also find Norton's equivalent circuit across the AB-terminals of same network from Thevenin's equivalent circuit.

(c) Consider the network shown in Fig. 4.

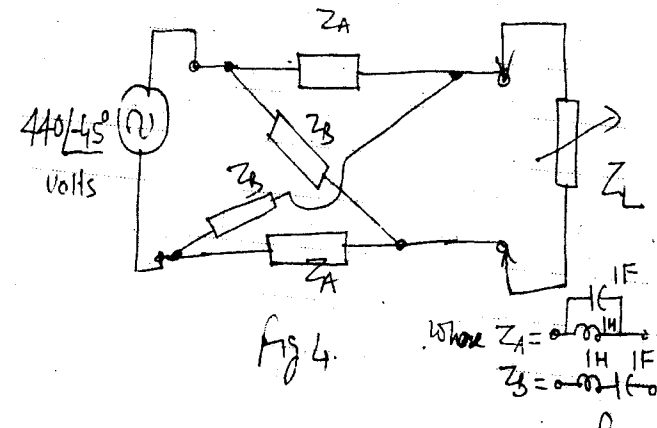


Fig. 4

- (i) What should be the value of Z_L for maximum power transfer from source to load in network shown in Fig. 4 ?
- (ii) What is the value of maximum power transfer from source to load in network shown in Fig. 4 ?

3. Answer any **two** parts of the following : (10×2=20)

- (a) What do you mean by "POLES" and "ZEROS" of a given network transfer function ? What are the significances and limitations of network transfer functions ? Explain the complex frequency in circuit theory.
- (b) Consider the network shown in Fig. 5.

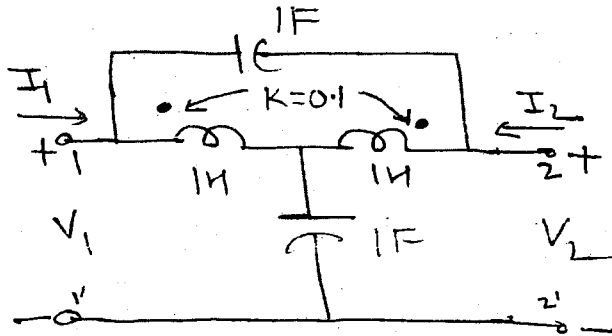


Fig. 5

Find $\frac{V_2}{V_1}$ for network shown in Fig. 5. Also draw and explain the pole zero diagram of $\frac{V_2}{V_1}$ and check its absolute stability of network.

- (c) Consider the network shown in Fig. 6.

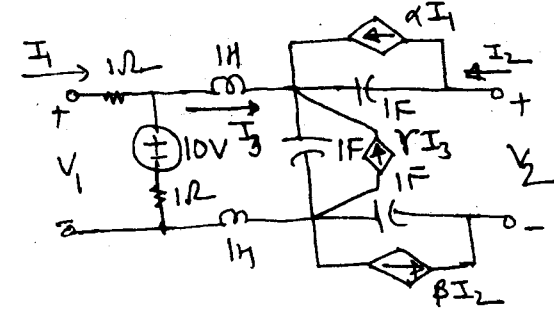


Fig. 6

- (i) Find $\alpha_{21}(s)$ & $G_{21}(s)$
- (ii) Find $Y_{12}(s)$ & $Z_{12}(s)$

4. Answer any **two** parts of the following : (10×2=20)

- (a) Consider the network shown in Fig. 7.

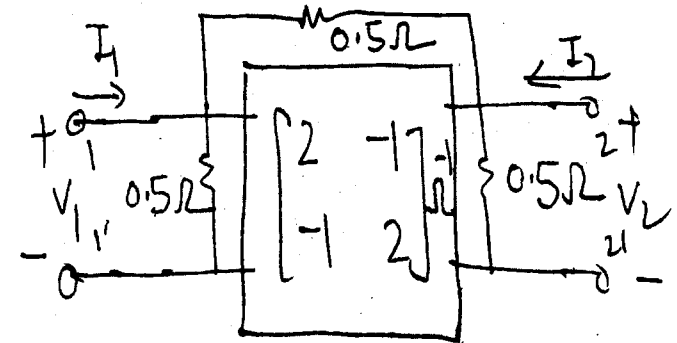


Fig. 7

- (i) Determine I_1 & I_2 in function of V_1 and V_2 .
(ii) Determine V_1 & V_2 in function of I_1 and I_2 .
(b) Consider the network equations shown in Fig. 8.

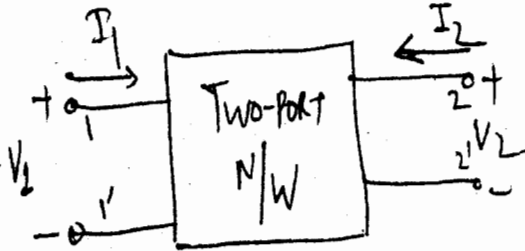


Fig. 8

Where

$I_1 = 5V_1 + V_2$
$I_2 = -V_1 + 5V_2$

Determine the [h] & [g]- parameters of two-port network shown in Fig. 8.

- (c) Consider the two-part network shown in Fig. 9.

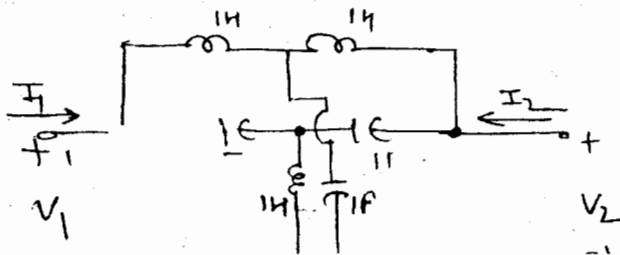


Fig. 9

Determine the [z] & [y]- parameters of two-port network shown in Fig. 9.

5. Answer any **two** parts of the following : (10×2=20)
(a) What do you mean by 'POSITIVE REAL FUNCTION' ? What are the properties associated with PRF ? What are the significances of PRF ?
(b) Consider the single port network as shown in Fig. 10.

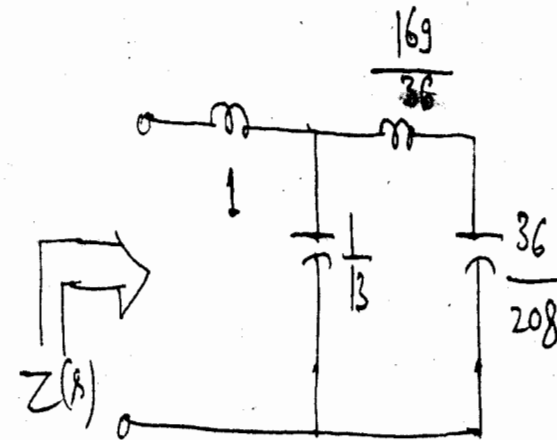


Fig. 10

- (i) Determine Foster Second forms.
(ii) Determine Cauer Second forms.
(c) (i) What do you mean by "ACTIVE" and "PASSIVE" filters ? What are the advantages and disadvantages of active filters over passive filters ? Discuss the different types of active and passive filters.

(ii) Consider the function $F(s)$ as follows :

$$F(s) = \frac{s^2 + \alpha s + \beta}{s^2 + \alpha' s + \beta'}$$

Where $\alpha, \beta, \alpha' \text{ \& } \beta' \geq 0$

What should be the conditions when $F(s)$ is PRF ?