

M TECH
(SEM-II) THEORY EXAMINATION 2017-18
MODELLING AND SIMULATION OF POWER ELECTRONIC CIRCUIT

Time: 3 Hours**Total Marks: 70****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 7 = 14**

- a Give an overview of PSPICE.
- b How does latch-up occur in an IGBT?
- c What is modeling of diode?
- d What is the role of POWERGUI in MATLAB?
- e Enumerate advantages of MATLAB SIMULINK software?
- f. What is the role of scope in MATLAB?
- g What do you understand by workspace?

SECTION B**2. Attempt any three of the following:****7 x 3 = 21**

- a. How simulation and design of AC voltage controller is done in MATLAB SIMULINK software?
- b. What are main types of Spice .Also write down the limitations of PSPICE?
- c. Explain the criteria for switch selection in detail.
- d. Explain Independent and Dependent DC sources.
- e. How to generate x and y co-ordinates of 100 equidistant points on a unit circle in MATLAB.

SECTION C**3. Attempt any one part of the following:****7 x 1 = 7**

- (a) Explain how modeling and simulation of any chopper circuit can be done using MATLAB SIMULINK software?
- (b) Explain Voltage controlled switch in PSPICE. How can an idealized MOSFET drive circuit in PSPICE be drawn?

4. Attempt any one part of the following:**7 x 1 = 7**

- (a) Explain switch selection in power electronics devices and also draw the switch implementation using a MOSFET and Diode.
- (b) Draw the model of Thyristor using NPN and PNP transistors in MATLAB.

- 5. Attempt any *one* part of the following:** **7 x 1 = 7**
- (a) Draw and Explain the modeling of MOSFET in MATLAB.
 - (b) Explain the major differences between PSPICE and MATLAB simulink software.
- 6. Attempt any *one* part of the following:** **7 x 1 = 7**
- (a) Design Transistor Snubber circuits and Thyristor snubber circuits using Pspice.
 - (b) Explain MOSFET and IGBTs Drive circuit in detail.
- 7. Attempt any *one* part of the following:** **7 x 1 = 7**
- (a) Draw the equivalent circuit using N-Channel MOSFET and PNP Bipolar Transistor.
 - (b) How the circuit diagram of over-voltage snubber can be drawn in MATLAB.