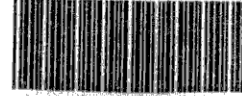


Printed Pages :6



*1991 *

426

NEE-101/NEE-201

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 199130

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B.Tech. (Semester-I)

SPL. THEORY EXAMINATION, 2014-15

BASIC ELECTRICAL ENGINEERING

Time : 3 Hours]

[Total Marks : 100

Note: Do as directed. Missing data if any may be suitably assumed and mentioned. Symbols have their usual meaning.

Section – A

1. Attempt all parts of this question. Each part carries two marks. 2×10=20
 - (a) Define unilateral and bilateral with examples.
 - (b) Three equal resistances of 5Ω are connected in star. Find the equivalent Delta.

199130]

(1)

[Contd...

- (c) Define polyphase circuit with suitable example and waveform.
- (d) Differentiate between deflection torque and controlling torque.
- (e) A series circuit has $R = 15\Omega$, $L = 0.15 \text{ H}$, $C = 5\mu\text{F}$. Calculate Resonant frequency of the circuit.
- (f) Define Flux density, reluctance and magnetic flux density.
- (g) Discuss necessity of Earthing.
- (h) What is the back emf in DC motor?
- (i) An induction motor having 8 poles runs at 800 rpm. If the supply frequency is 50 Hz, find slip.
- (j) What are the types of transformer? Explain with suitable diagram and definition.

Section – B

2. Attempt any three parts of this question. Each part carries 10 marks: 10×3=30

- (a) (i) Determine current in 15Ω resistance using Thevenin's theorem and verify the same by Norton's theorem shown in figure-1.

- (b) Write in detail about Slip-Torque Characteristics for three phase Induction Motor with proper diagram.
- (c) Explain two wattmeter method in any star connection or Delta connection with neat diagram and phasor diagram.

—x—

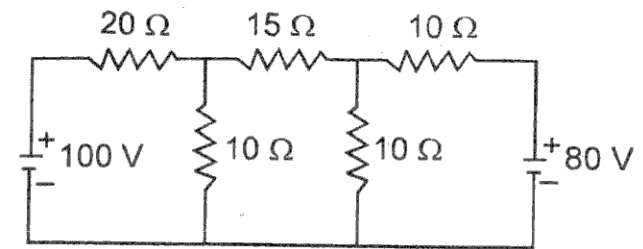


Figure-1

- (ii) State and prove maximum power transfer theorem.
- (b) (i) Prove that in a pure capacitor circuit average power is zero.
- (ii) Give the expression for bandwidth and show the following result $Fr = \sqrt{f1 \times f2}$
- (c) Describe with neat diagram the principle and working of moving iron instruments.
- (d) (i) Derive the relation between line voltage and phase voltage in balanced star connection.
- (ii) Derive the relation between line voltage and phase voltage in balanced delta connection.
- (e) Explain the frequency curve in a series R-L-C circuit with proper labeling.

Section – C

Note: Attempt all questions of this part. Each question carries 10 marks. $5 \times 2 \times 5 = 50$

3. Attempt two parts of this question:

- (a) Derive Star-delta transformation.
- (b) Find the resultant voltage of the following $v_1 = 25 \sin \omega t$, $v_2 = 10 \sin(\omega t + \pi/6)$, $v_3 = 30 \cos \omega t$, $v_4 = 20 \sin(\omega t - \pi/4)$.
- (c) Explain source transformation.

4. Attempt two parts of this question.

- (a) Derive the relation for Q-factor of the series R-L-C circuit.
- (b) An impedance of $(8+j7)$ is connected with $(3-j4)$ in parallel, then further is connected with $(5+j3)$ in series with supply of 100 v, 50 Hz. Draw the circuit diagram and hence find the current in circuit and total impedance of the circuit.
- (c) Explain the series R-L circuit with phasor diagram, power triangle, and voltage triangle.

5. Attempt any two parts of this question :

- (a) Derive the emf equation of transformer.
- (b) Give the analogy between magnetic and electric circuit. Also give the brief of B-H curve.
- (c) A wrought iron bar 30 cm long and 5 cm diameter is bent into a circular shape. It is then wound with 500 turns of wire. Calculate the current required to produce a flux of 0.5 milli weber in magnetic circuit. Assume permeability of iron is 3000.

6. Attempt any two parts of this question :

- (a) Derive the back emf of motor, also find the torque equation of the motor.
- (b) Why earthing is necessary? Explain the types of proper connection to earthing.
- (c) Define power factor. What are the measures used to improve the power factor?

7. Attempt any two parts of this question :

- (a) Why single Phase Induction Motor is not self starting? Give the various methods to start. Explain any two of them with proper diagram and phasor diagram.