



Printed Pages : 7

TEE – 101/201

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 2018/2019**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech. (Sem. I & II)**

**SPECIAL CARRYOVER EXAMINATION, 2006-07**

**ELECTRICAL ENGINEERING**

*Time : 3 Hours]*

*[Total Marks : 100*

- Notes :*
- (1) Answer **all** the **five** questions.*
  - (2) All questions carry **equal** marks.*

**1** Answer any **four** parts out of the following : **5×4=20**

- (a) A circuit consists of three parallel branches.  
The branch currents are represented by

$$i_1 = 10 \sin(\theta - 45^\circ)$$

$$i_2 = 15 \cos \theta$$

$$i_3 = 20 \sin(\theta + 60^\circ)$$

Find the resultant current and express it in the form  $i = I_m \sin(\omega t \pm \alpha)$  and draw the phasor diagram.

- (b) A coil has an inductance of 19 mH and a resistance of 8 ohm. It is connected to a sinusoidal supply of 200 V, 50 Hz.


**Z-2018/2019]**

**1**

**[Contd...**

*Calculate*

- (i) the impedance
  - (ii) the supply current
  - (iii) the power factor
  - (iv) the power consumed
  - (v) the reactive volt-ampere.
- (c) For the circuit shown in **fig. 1**, calculate
- (i) the equivalent impedance
  - (ii) the supply current
  - (iii) the supply power factor

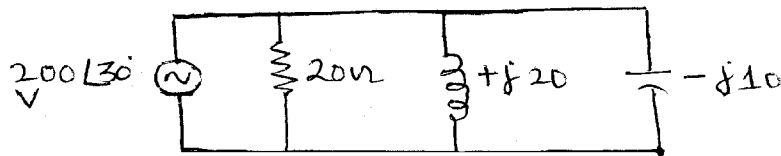


**Fig. 1**

- (d) Explain the terms "Resonant frequency", "Quality factor" and "Bandwidth" related to a series R-L-C a.c. circuit. How are these terms related to each other ? What is the significance of high Q-factor ?
- (e) A coil of resistance 50 ohm and inductance 0.5 H is connected in parallel with a capacitor of  $100 \mu F$ . Calculate the frequency at which the circuit acts as a non-inductive resistance using basic concept. Calculate the value of this non-inductive resistance and the bandwidth.

- (f) Explain analogy between magnetic circuit and electric circuit. How does magnetic circuit differ from the electric circuit ?


2 Answer any **four** parts out of the following : **5×4=20**

- (a) State and explain Norton's theorem. Why is it called dual of Thevenin's theorem ?
- (b) Using star-delta transformation, determine the current and power supplied by the battery in the circuit shown in **fig. 2**.

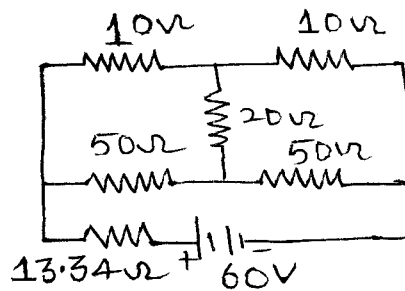


**Fig. 2**

- (c) Determine current in all branches of the circuit shown in **fig. 3** using Superposition theorem.

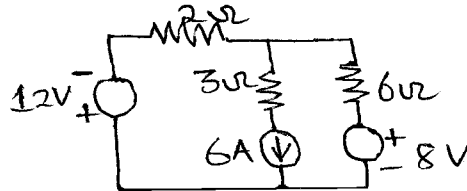

**Fig. 3**

- (d) Calculate the value of  $R$  which will absorb maximum power from the circuit shown in **fig. 4**. Also calculate the maximum power absorbed in  $R$ .

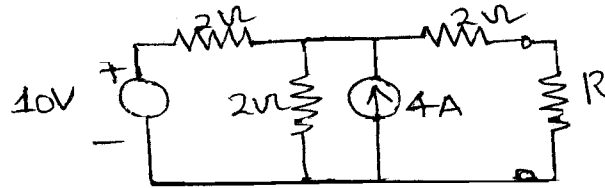

**Fig. 4**

- (e) Why does induction type energy meter read energy while induction type wattmeter read power ?

An energy meter is designed to make 100 revolutions of the disc for one unit of energy. Calculate the number of revolutions made by it when connected to a load taking 50 A at 250 V and 0.8 power factor for an hour.

If it actually makes 980 revolutions, find the percentage error.

- (f) Explain construction and principle of operation of attraction type moving iron instrument. Why is its scale not uniform ?

**3** Answer any **two** parts out of the following : **10×2=20**

- (a) Discuss advantages of three phase systems.

Three identical impedances having a resistance and a capacitance are connected in a delta across a 3-phase, 400 V, 50 Hz supply. The power input to the load is measured by two wattmeter method. The readings of the two wattmeters are 6000 W and 2400 W. Determine

- (i) the power factor of the circuit
- (ii) the line current
- (iii) the resistance and capacitance of each phase.

- (b) Explain principle of operation of a transformer. Derive e.m.f. equation of a single phase transformer.

- (c) Open and short circuit tests on a 4 kVA, 200 V/400 V single phase transformer gave the following results :

O.C. test (on L.V. side) : 200 V, 2 A, 100 W

S.C. test (on H.V. side) : 400 V, 10 A, 200 W

Determine the efficiency and voltage regulation of the transformer at full load and 0.8 power factor lagging.

**4** Answer any **two** parts out of the following : **10×2=20**

- (a) Explain principle of electromechanical conversion. Draw power flow diagrams for motor and generator.
- (b) What are various methods of speed control of d.c. separately excited motor ? Explain in brief.
- (c) A d.c. shunt motor draws 82 A at 220 V on full load. The armature and field resistances are 0.2 ohm and 110 ohm respectively. The stray losses are 600 W. Determine
  - (i) Constant losses and full load copper losses
  - (ii) Output power and overall efficiency
  - (iii) The maximum efficiency.

**5** Answer any **two** parts out of the following : **10×2=20**

- (a) Explain principle of operation of a three phase induction motor. What is meant by 'slip' ? Derive an expression for frequency of rotor currents.
- (b) Draw and explain slip-torque characteristics of a three phase induction motor and show the effects of
  - (i) Varying rotor resistance
  - (ii) Supply voltage. State the operating conditions when the slip is
  - (iii) Negative
  - (iv) Positive, greater than one.

**Z-2018/2019]**

**6**

**[Contd...**

- (c) Explain following methods of starting of a single phase induction motor
- (i) Capacitor start capacitor run method
  - (ii) Permanent-split capacitor method.
-