

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 199129

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech. (End Sem.)

SPL. THEORY EXAMINATION 2014-15

ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 100

Note: Attempt questions from all sections as per instructions.

Section - A

1. This question consists of short answer questions. Attempt all parts of this question. All parts carry equal marks.

(2×10=20)

- (a) What do you mean by Doping? Describe its need.
- (b) Give all the Equivalent / Approximation circuits of a Diode.
- (c) Differentiate between Clipper and Clamper circuit.

- (d) Describe the equivalent circuit of a Transistor.
- (e) Why the Q-point varies in transistors?
- (f) Differentiate between Depletion and Enhancement type MOSFET.
- (g) Define Threshold Voltage for an E-MOSFET. Also define I_{DSS} for an JFET.
- (h) Draw the Drain V-I characteristics of n channel JFET.
- (i) Differentiate between N-type and P-type semiconductor.
- (j) Draw npn CE transistor in active region.

Section - B

2. Attempt any three parts of this question. All parts carry equal marks. (10×3=30)

- (a) Compare different types of rectifier, giving their circuit.
- (b) (i) Describe the working of voltage multiplier circuit.
(ii) Define / explain the following:
 - (a) Slew Rate
 - (b) Threshold Voltage
 - (c) Ripple Factor

6. Attempt any two parts of this question :

- (a) Describe measurement of Voltage, Frequency & Phase using CRO.
- (b) Describe the working of Digital Milimeter giving their block diagram.
- (c) Describe the working of Digital Voltmeter giving their block diagram.

7. Attempt any one part of this question :

- (a) Define amplitude modulation. Write the expression of AM wave. Define modulation index for AM wave.
- (b) Explain any one demodulation technique of AM wave.
- (c) Give comparison between FM and PM wave.

* * *

(d) CMRR

(e) Pinch off Voltage

- (c) (i) Show the biasing arrangement for the NPN CE configuration so that it works in active region. Describe characteristics for CE configuration. Label all variables and also indicate the regions.

- (ii) Explain the basic construction, operation and characteristics of LED.

- (d) Explain the construction, operation and characteristics of n- channel JFET.

- (e) (i) Describe the characteristics of Op- amp. Also give its symbol and equivalent circuit.

- (ii) A half wave rectifier is used to supply 10 V to a resistive load of 400 ohm. If the diode has a forward resistance of 20 ohm, determine the value of ac voltage supplied to the circuit.

Section - C

Note: Attempt all questions of this section. All questions carry equal marks. (10×5=50)

3. Attempt any two parts of this question.

- (a) Draw and explain the V-I characteristic of a P-N

Junction diode. Also describe the effect of Temperature on the V-I characteristic of a P-N Junction diode.

- (b) Draw the output waveform for the circuit of Figure 3.b.

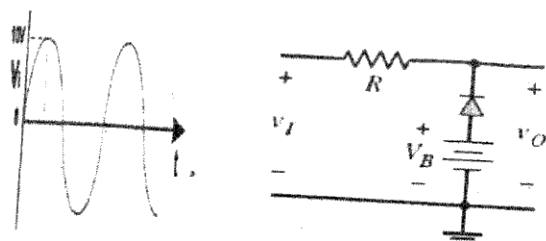


Fig. 3.b.

- (c) Describe Varactor and Tunnel diode. Also draw their symbol.

4. Attempt any two parts of this question.

- (a) Describe the construction of a NPN transistor. Define α and β with respect to BJT and derive the relationship between them.

- (b) Refer the information appearing in Fig.4.b. Determine $I_C, V_E, V_C, I_B, & V_{CE}$. assume $\beta = 100$.

- (c) Explain the construction and working of E-MOSFET.

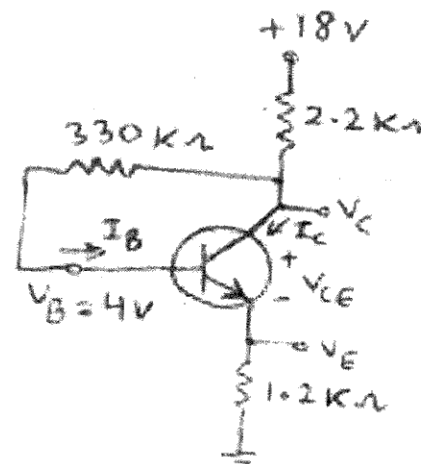


Fig.4.b.

5. Attempt any two parts of this question.

- (a) Draw the circuit of Integrator using op-amp and obtain expression for output.

- (b) Find the output V_O for the circuit of Fig 5.b in terms of V_1 and V_2 .

- (c) Explain four types of Negative Feedback configuration for an Op-amp.

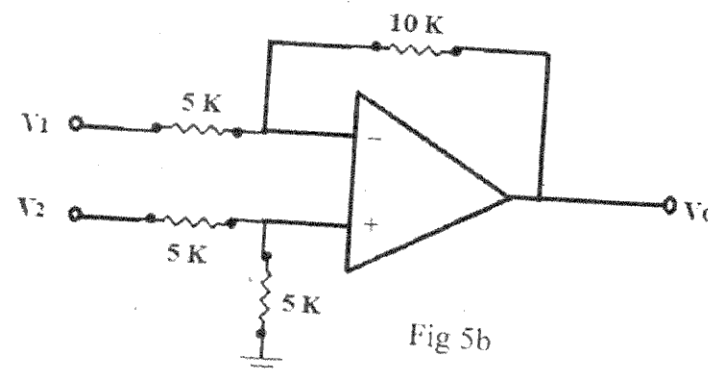


Fig 5b