

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0321

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. III) THEORY EXAMINATION 2011-12

ANALOG AND DIGITAL ELECTRONICS

Time : 3 Hours

Total Marks : 100

Note :- (1) Answer **all** questions.

(2) All questions carry equal marks.

1. Attempt any **four** parts of the following : **(5×4=20)**
- (a) Explain the working of tunnel diode. Enlist its applications.
 - (b) Discuss how the variable capacitance is achieved in varactor diode. Enlist the application of varactor diode.
 - (c) Define "Dark current" in photodiode. Why photodiode is always used in reverse bias conditions ?
 - (d) Explain the principle and working of light emitting diode (LED) with V-I characteristic.
 - (e) How the construction of the Schottky barrier diode is different from conventional semiconductor diode significantly and describe its mode of operation.
 - (f) Explain the working of transistor as switch.

2. Attempt any **two** parts of the following : **(10×2=20)**
- Draw the equivalent circuit of BJT at high frequency and derive the expression for upper cut-off frequency.
 - Discuss the higher and lower frequency response of RC coupled amplifier. Explain the effect of coupling and bypass capacitor on the bandwidth of an amplifier.
 - List five characteristics of an amplifier, which are modified by negative feedback. Derive expression for the effective input and output resistance of current series feedback topologies.

3. Attempt any **two** parts of the following : **(10×2=20)**
- What are the Barkhausen conditions required for sustained sinusoidal oscillation ? Sketch the circuit of a Wein bridge oscillator and derive the expression for frequency of oscillation.
 - Explain with the circuit diagram the working of a transistor RC phase shift oscillator and derive the condition for sustained oscillations.
 - Discuss how does the circuit of a Clapp oscillator differ from that of a Colpitt oscillator.
 - Explain the properties of a quartz crystal which are responsible for its use in an oscillator.

4. Attempt any **two** parts of the following : **(10×2=20)**
- Sketch the circuit diagram for universal shift register and explain its working.
 - Implement the following Boolean function using 8×1 multiplexer :

$$F(A,B,C,D) = \sum m(2,4,5,7,10,14).$$
 - Design a four bit synchronous up counter using J-K flip flop.
 - Explain the working of SR flip flop using NAND gates.
 - Discuss Race around condition of J-K flip flop. Show how this condition can be removed.

5. Attempt any **two** parts of the following : **(10×2=20)**
- Design and explain a circuit diagram for astable multivibrator having 50% duty cycle using IC 555.
 - Enlist the various types of analog to digital (A/D) converter. Explain the operation of R-2R ladder type digital to analog (D/A) converter with a neat sketch.
 - Write short notes on the following :
 - Series type voltage regulator
 - Sequential memory.