

B TECH
(SEM-III) THEORY EXAMINATION 2018-19
SWITCHING THEORY & LOGIC DESIGN

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt *all* questions in brief.

2 x 10 = 20

- What is race around condition in JK flip-flop?
- Differentiate between EPROM and EEPROM.
- Design full adder using two half adders.
- Determine the value of base x if:
 - $(211)_x = (152)_8$
 - $(193)_x = (623)_8$
- What are hazards?
- A logical expression in the standard SOP form is as under:


$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$$
 Minimize it using the k-map technique.
- Explain the difference between PLA and PAL.
- Distinguish Encoder and Decoder?
- How is the capacity of a PLA specified?
- Differentiate between multiplexer and demultiplexer.

SECTION B

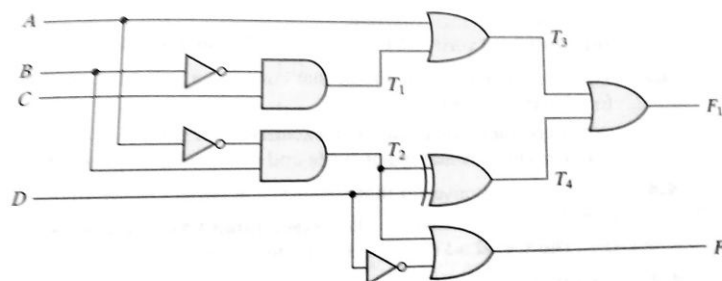2. Attempt any *three* of the following:

10 x 3 = 30

- Minimize the following logic function k-map and verify the answer using the Quine-McCluskey method $Y(A,B,C,D) = \sum m(0,1,2,3,6,7,8,10,12,13)$
- What is multiplexer? Design 16:1 multiplexer using 4:1 multiplexer?
- Consider the combinational circuit shown in figure



- Derive the Boolean expression for T_1 to T_4 . Evaluate the output F_1 and F_2 .
 - Derive the truth table with 16 binary combination of the four input variable.
- Convert a D flip flop into (i) T-flip flop (ii) JK flip flop?
 - What do you mean by hazard? Give the classification and Explain in detail.

SECTION C

3. **Attempt any *one* part of the following:** **10x 1 = 10**
- a) Simplify the given function using k-map
- $$F(a,b,c,d) = \Sigma(0,1,3,4,6,8,10,11)$$
- b) Generate the 7-bit hamming code for given data 1011.
4. **Attempt any *one* part of the following:** **10x 1 = 10**
- a) Construct a BCD to excess 3 code converter with a 4-bit adder. What must be done to change the circuit to an excess 3 to BCD code converter?
- b) What is magnitude comparator? Design a three-bit comparator circuit using logic gates.
5. **Attempt any *one* part of the following:** **10x 1 = 10**
- a) Differentiate between asynchronous counter and synchronous counter? Design and implement Two-Bit-Ripple up-counter using positive edge-triggered J-K Flip-flop.
- b) Differentiate between Flip flop and latch? Convert SR Flip flop in to D flip flop.
6. **Attempt any *one* part of the following:** **10x 1 = 10**
- a) Differentiate between asynchronous and synchronous sequential circuit. Also design MOD 5 asynchronous counter using JK flip flop.
- b) Write short notes on any two of the following
- (i) Critical and non critical race
 - (ii) Cycle
 - (iii) Debounce circuit
7. **Attempt any *one* part of the following:** **10x 1 = 10**
- a) Implement the following function using PLA.
- $$A(x,y,z) = \Sigma m(1,2,4,6)$$
- $$B(x,y,z) = \Sigma m(0,1,6,7)$$
- $$C(x,y,z) = \Sigma m(2,6).$$
- b) Discuss the different types of RAM and ROM?