



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131501

Roll No. 

--	--	--	--	--	--	--	--	--

**B.Tech. (Semester-V)****(SPL.) THEORY EXAMINATION, 2014-15  
INTEGRATED CIRCUITS****Time : 3 Hours]****[Total Marks : 100****Note:** All questions are compulsory and carry equal marks.1. Attempt any four parts. All parts carry equal marks.

5×4=20

- (a) What are the desirable characteristics of current mirror circuits. Draw the simple BJT current mirror and obtain the expression for current transfer ratio using matched transistors.
- (b) Explain the circuit of Wilson MOS current mirror. Also discuss how it can be improved.
- (c) The parameter of the three transistor CM are  $V_{CC} = 9\text{ V}$ ,  $V_{EE} = 0$ ,  $R_1 = 12\text{ K}\Omega$ ,  $V_{BE(on)} = 0.7\text{ V}$ ,  $\beta = 75$ ,  $V_A = \infty$ . Calculate the value of current,  $I_{ref}$ ,  $I_0$ ,  $I_{C1}$ ,  $I_{B1}$ ,  $I_{B2}$ ,  $I_{B3}$ ,  $I_{E3}$ .

131501]

(1)

[Contd...

- (d) What is the need for compensating base current of bipolar mirror?
- (e) Describe the operation and characteristics of a BJT complementary push-pull output stage.
- (f) Describe what is meant by output short circuit protection.
2. Attempt any two questions. All questions carry equal marks:  $10 \times 2 = 20$
- (a) Compare and contrast active filters and passive filters. Design a second order low Pass Butterworth filter to have cut-off frequency of 1 KHz.
- (b) Derive the expression of voltage gain in KHN Biquad Filter. Draw the KHN Biquad filter and derive transfer function of the BPF and LPF from that.
- (c) (i) Draw the V-I converter and derive its output equation for grounded load.
- (ii) Derive the output expression for RC Phase Shift Oscillator.
3. Attempt any two questions. All questions carry equal marks:  $10 \times 2 = 20$
- (a) Realize the circuit of 2 input NOR gate and 2 input NAND gate using CMOS and explain the operation.
- (b) Give CMOS implementation of a SR flip-flop and explain its working.

- (c) Discuss the features of CMOS circuit. Realize one AND-OR-INVERT (AOI) and one OR-AND-INVERT (OAI) function using CMOS logic circuit.
4. Attempt any two questions. All questions carry equal marks:  $10 \times 2 = 20$
- (a) Draw and explain the working of monostable multivibrator using op-amp.
- (b) What are precision rectifiers? Describe the working of single op-amp based full wave precision rectifier.
- (c) What do you mean by the quadrant operation of multiplier? Draw and explain a GILBERT analog multiplier.
5. Attempt any two questions. All questions carry equal marks:  $10 \times 2 = 20$
- (a) Draw the block diagram of a PLL and explain its operation. Explain lock-in-range, capture range and pull-in time of a PLL. List the application of PLL.
- (b) Explain the operation R-2R Ladder D/A Converter.
- (c) Design a 555 timer as a stable multivibrator giving its block diagram which provide an output signal frequency of 2 KHz and 75% duty cycle.

—x—